

Class:	CPE100L - 1002	Semester:	Spring 2020
Points		Document author:	Kristy Nguyen
		Author's email:	nguyek20@unlv.nevada.edu
		Document topic:	Postlab 10
Instructor's comments:			

## 1. Introduction / Theory of Operation

Lab 10 is about sequential circuit design, where we design a simple counter circuit and implement the circuit. In this lab, we will design a 4-bit sequential counter with preset and reset input.


## 2. Prelab Report

My prelab report will be attached with the submission.

## 3. Results of the Experiments


Exp.	Experiment Results
1	<p>a. Schematic</p>

## b. Simulation waveform(s)

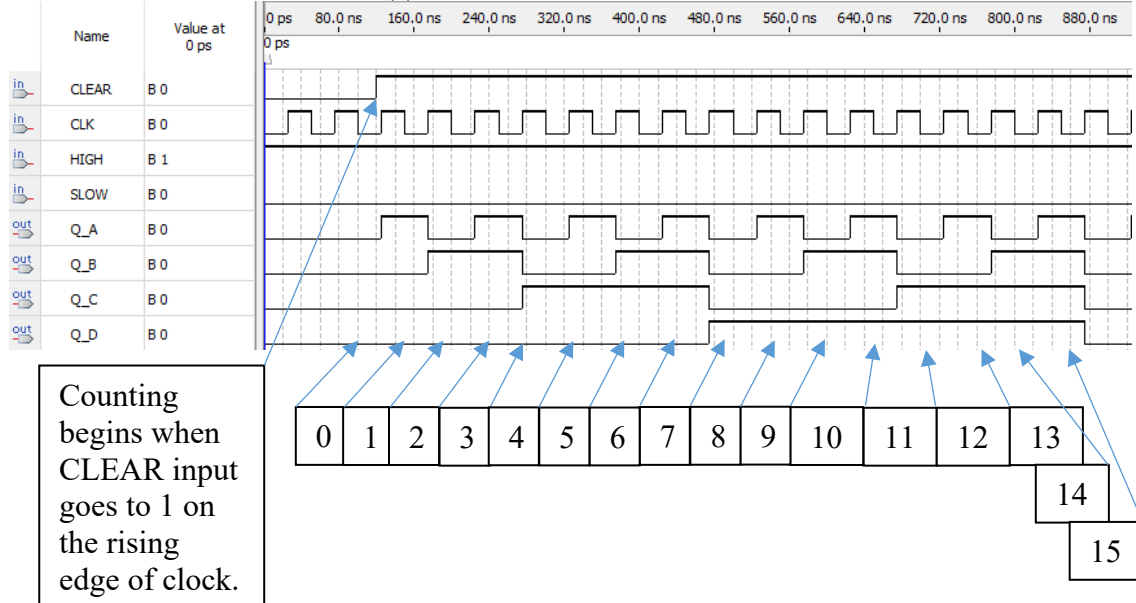


2

## a. Schematic

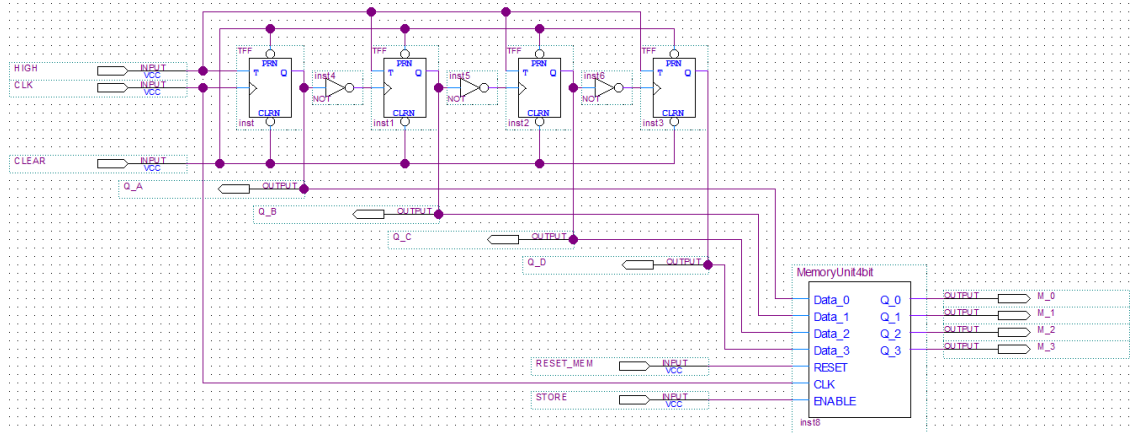



### b. Simulation waveform(s)

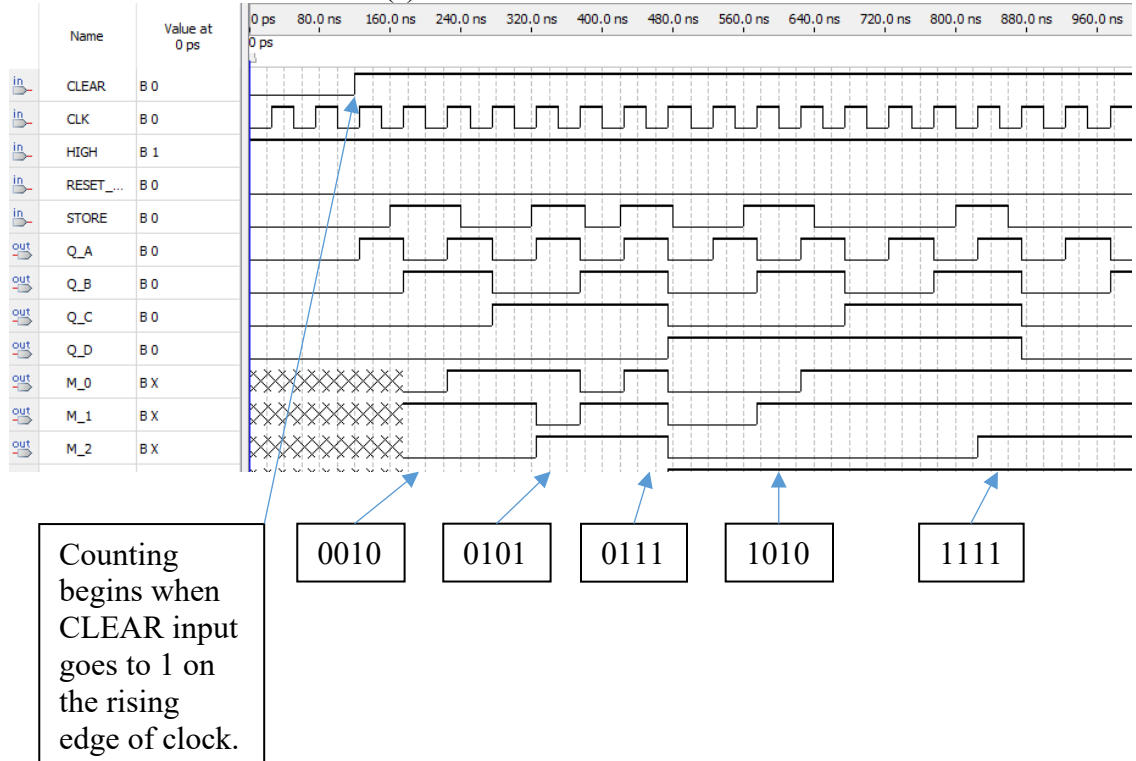

3

### a. Schematic

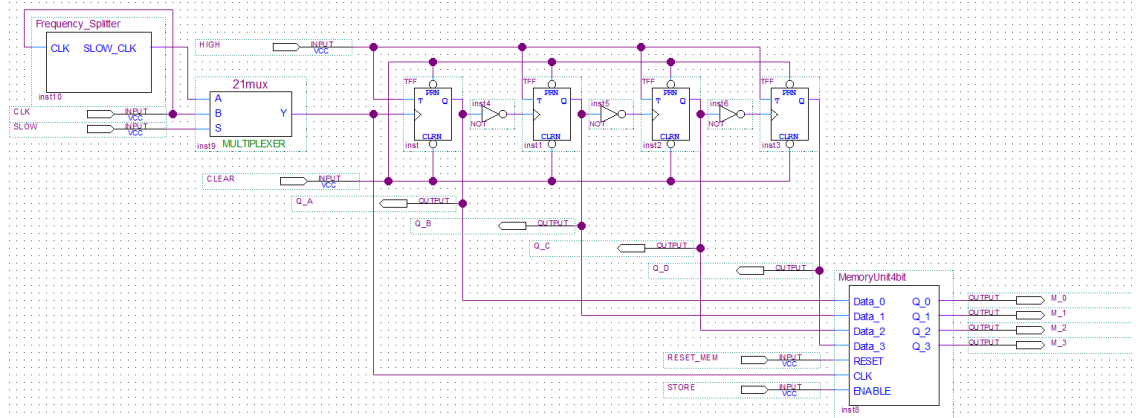


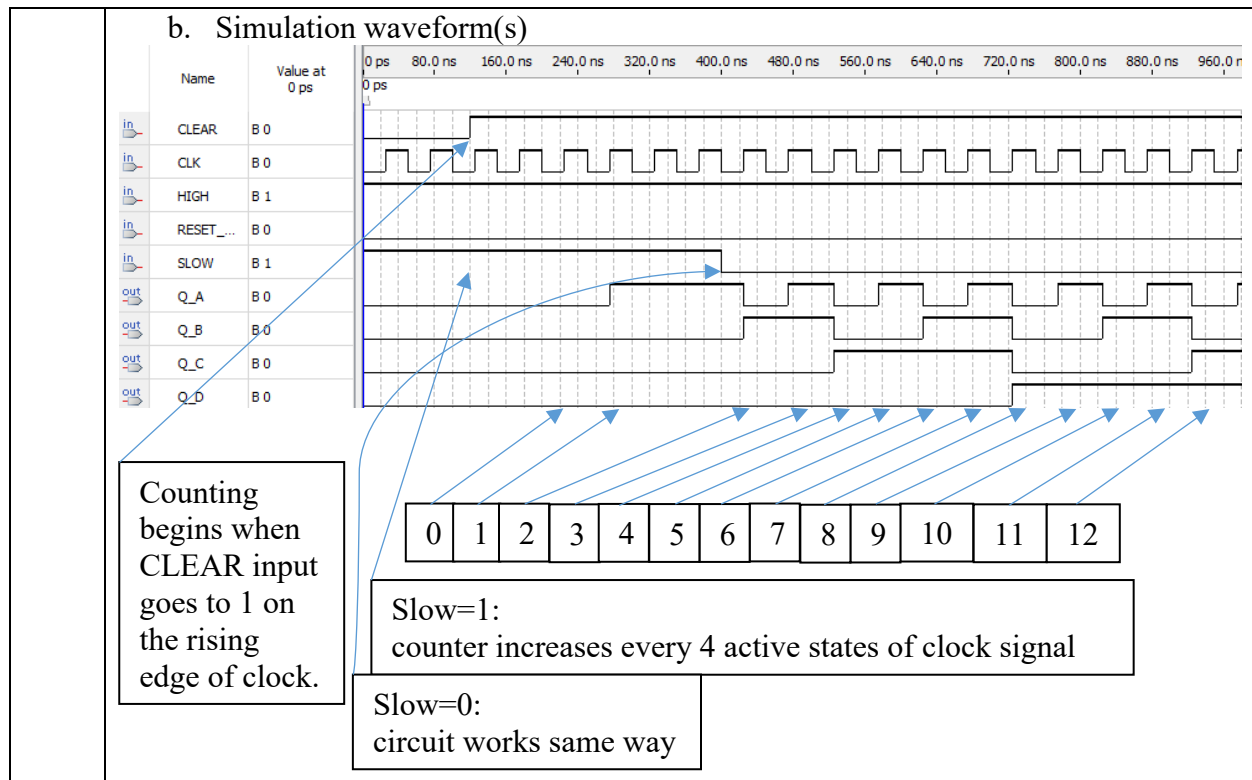

#### 4. Answer the questions

- 3 examples of counters in home electronics are ovens, washing machines, and microwaves. These home electronics use time measurement or calculates the time in timers.

2.

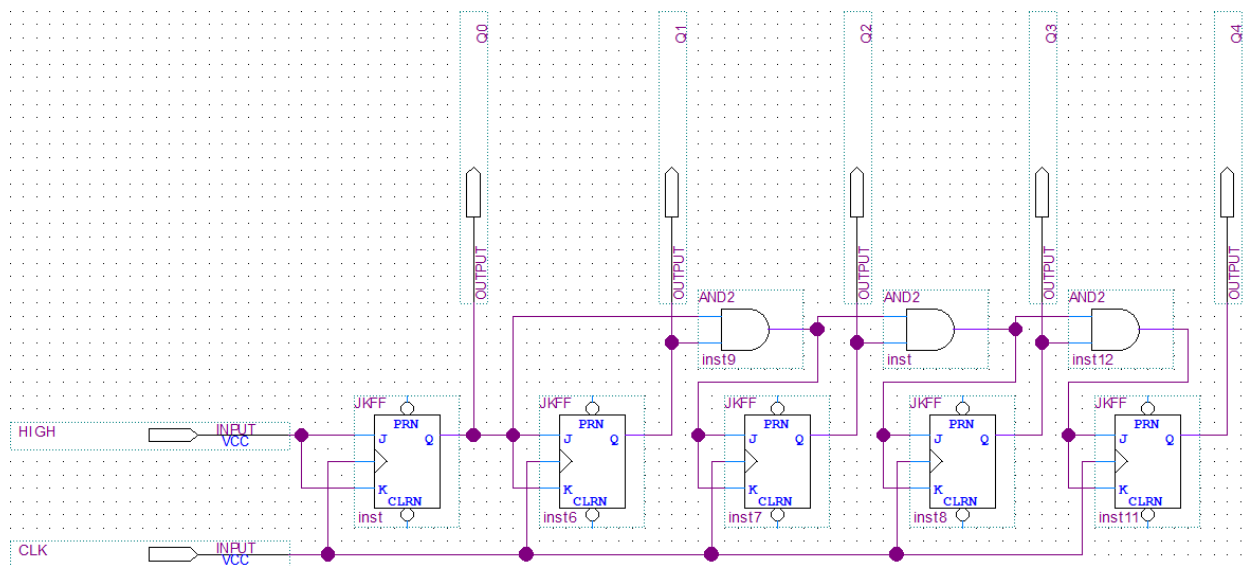

- 3 examples of counters that count other than 1, 2, 3... are up/down counters, decade counter, and modulus counter.

## **5. Conclusions**

This lab was fairly straightforward and much simpler than the other labs. Thanks to Smit's helpful description, I was able to successfully complete experiment 3 with a thorough understanding. The problem I had was how to make a frequency splitter, but Smit's explanation definitely helped me out. I learned that a frequency splitter can change the output for every 4 or other number of active states of clock signals. My knowledge of memory bits are strengthened for each time that I use the memory bit unit to store numbers.